

Electrical Circuits Lab. 0903219

Series RLC Resonance Circuit

- Series RLC Circuit Resonance Frequency f_r :

* The definition of the resonance frequency f_r is that it is the operating frequency that makes an **RLC** circuit a resistive circuit which means the imaginary part of the total impedance Z becomes zero.

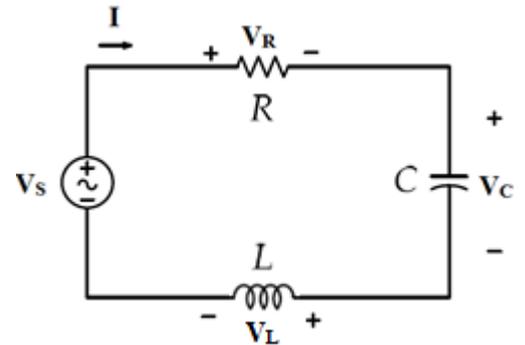


Figure (1) Series RLC circuit

* Depending on the above, we can find a formula for f_r by following the steps shown below:

When $f = f_r$ in a series RLC circuit,

$$\begin{aligned} \text{Im}\{Z\} &= 0 \\ \text{Im}\left\{R + j\omega rL + \frac{1}{j\omega rC}\right\} &= 0 \\ j\omega rL + \frac{1}{j\omega rC} &= 0 \\ \rightarrow j\omega rL &= \frac{-1}{j\omega rC} \rightarrow \omega r^2 = \frac{1}{LC} \\ \rightarrow \omega r &= \frac{1}{\sqrt{LC}} \rightarrow f_r = \frac{1}{2\pi\sqrt{LC}}. \end{aligned}$$

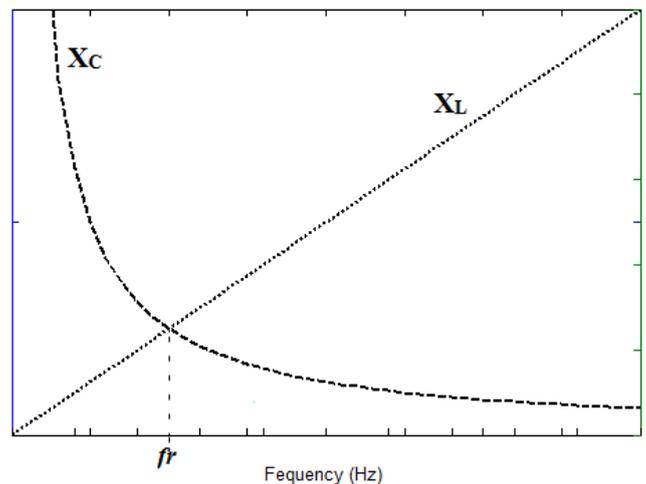


Figure (2) Frequency Response Curves for X_C and X_L reactance.

* Figure (2) shows important plot of how capacitor impedance X_C and inductor impedance X_L change with frequency and the place of f_r on the plot (in this case when X_C equal X_L).

- Simple steps to draw phasor diagram of a series RLC circuit without memorizing! and important conclusions:


* Start with the quantity (voltage or current) that is common for resistor R , capacitor C , and inductor L , which is here the source current I (because it passes through all of them without being divided).

Step1



* Now, we know that I and resistor voltage V_R are in phase or have the same phase angle (also in time domain we see that their zero crossings are the same on the time axis) and V_R is greater than I in magnitude.

Step2

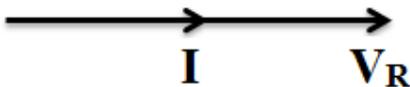

* Since I equal capacitor current I_C and equal inductor current I_L , and we know that I_C leads capacitor voltage V_C by 90 degrees and I_L lags inductor voltage V_L by 90 degrees, both V_L and V_C will be on the imaginary axis, and the phasor diagram of a series RLC circuit will have three cases depending on the source operating frequency f :

a- Case 1: $f = f_r$

As mentioned before when $f = f_r$ $X_L = X_C$ so $V_L = V_C$ and they are equal in magnitude and out of phase so V_C and V_L will cancel each other's effect and the circuit becomes a **resistive circuit** and the phase shift Θ equal zero (remember that $\Theta = \angle I = - \angle Z$), the value of **current I is maximum and equals V_S/R** and impedance **Z is minimum and equal R** .

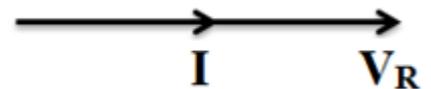


Figure (3) Series RLC Circuit Pharos Diagram when $f = f_r$

b- Case 2: $f < f_r$

Referring to Figure (2) notice that when $f < f_r$ $X_C < X_L$ so $V_C > V_L$ and the circuit becomes a **capacitive circuit**, which means that **I leads V_S and Θ is a positive angle (with respect to V_S)**.

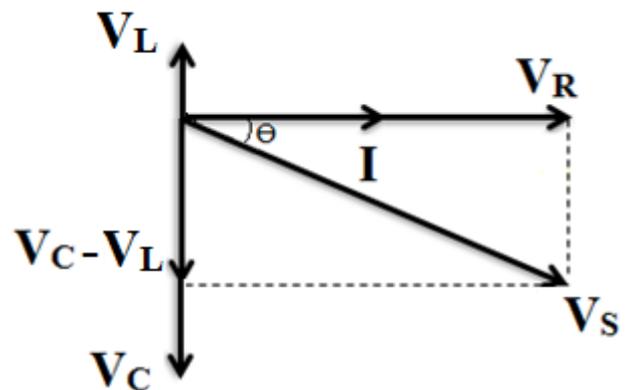


Figure (4) Series RLC Circuit Pharos Diagram when $f < f_r$

From its phasor diagram in figure (4) we can conclude the following:

1- $|V_S| = \sqrt{(|V_C| - |V_L|)^2 + |V_R|^2}$

2- $\Theta = \tan^{-1} \frac{|V_C| - |V_L| \text{ (imaginary part of } V_S)}{V_R \text{ (real part of } V_S)}$

and remember that $\Theta = \angle I = - \angle Z = - \tan^{-1} \frac{X_C - X_L \text{ (imaginary part of } Z)}{R \text{ (real part of } Z)}$

3- $|V_C|$ and $|V_L|$ can exceed the source voltage but $|V_C| - |V_L|$ and $|V_R|$ cannot.

c- Case 3: $f > fr$

Referring to Figure (2) notice that when $f > fr$ $X_L > X_C$ so $V_L > V_C$ and the circuit becomes an **inductive circuit**, which means that **I lags V_S and Θ is a negative angle (with respect to V_S)**.

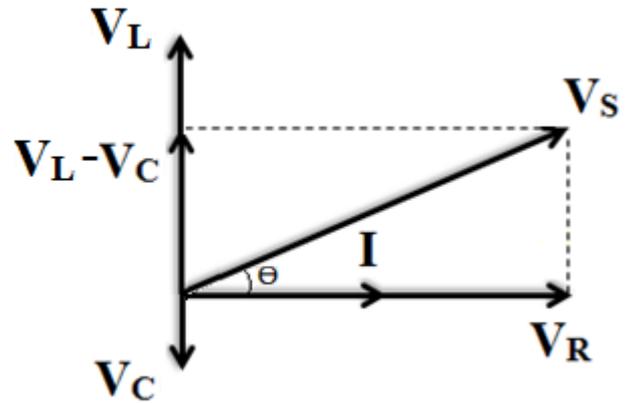


Figure (5) Series RLC Circuit Phasor Diagram when $f > fr$

From its phasor diagram in figure (5) we can conclude the following:

1- $|V_S| = \sqrt{(|V_L| - |V_C|)^2 + |V_R|^2}$

2- $\theta = \tan^{-1} \frac{|V_L| - |V_C| \text{ (imaginary part of } V_S)}{V_R \text{ (real part of } V_S)}$

and remember that $\theta = \angle I = - \angle Z = - \tan^{-1} \frac{X_L - X_C \text{ (imaginary part of } Z)}{R \text{ (real part of } Z)}$

3- $|V_C|$ and $|V_L|$ can exceed the source voltage but $|V_L| - |V_C|$ and $|V_R|$ cannot.

- How the circuit quantities change with frequency:

* Figure (2) and the circuit phasor diagram helps in finding the circuit quantities change with voltage source frequency f changing.

* As shown in figure (2), at low frequency f the difference between X_C and X_L is huge but with f increasing this difference starts to decrease so Z will decrease until f reaches fr where Z becomes minimum, after f exceeds fr , the difference between X_C and X_L increases with frequency increasing so Z will increase. In a concise way, the total impedance Z will decrease before f reach fr then increase when f exceeds fr and it's value is minimum at resonance frequency and equals R as shown in figure (6).

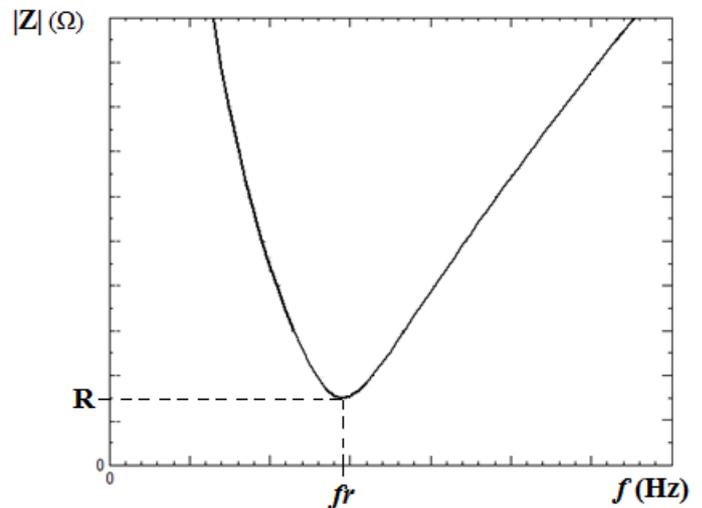


Figure (6) $|Z|$ vs. f

* Θ ranges from -90° to 90° ($-90^\circ < \Theta < 90^\circ$). And since $|\theta| = \tan^{-1} \frac{|X_L - X_C|}{R}$ and the \tan^{-1} function is increasing on the interval from -90° to 90° , the phase shift Θ (or the current angle $\angle I$) will decrease before f reach fr then increase when f exceeds fr and it's value is minimum at resonance frequency and equals **zero** as shown in figure (7).

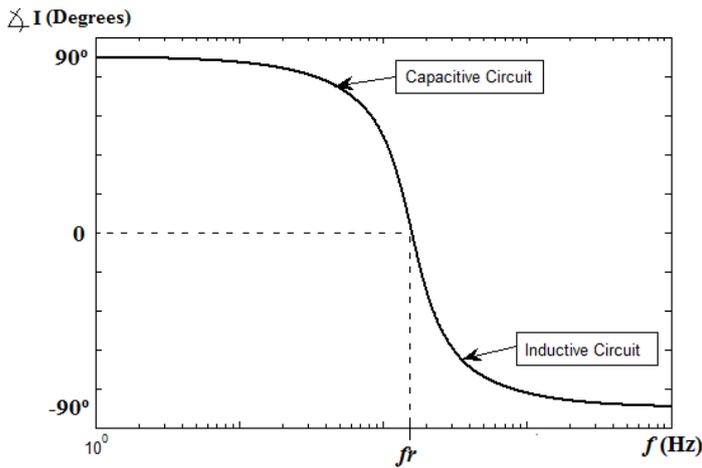


Figure (7) Θ vs. f

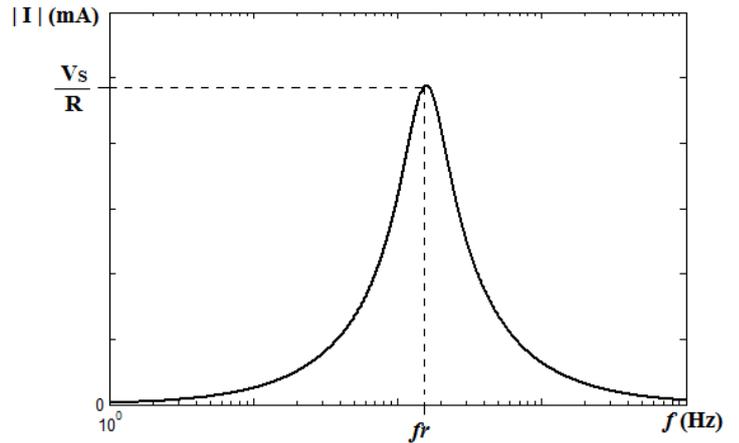


Figure (8) $| I |$ vs. f

* Because I is inversely proportional to Z , the total current I will increase before f reaches f_r then decrease when f exceeds f_r and it's value is maximum at resonance frequency f_r and equals V_s/R as shown in figure (8).

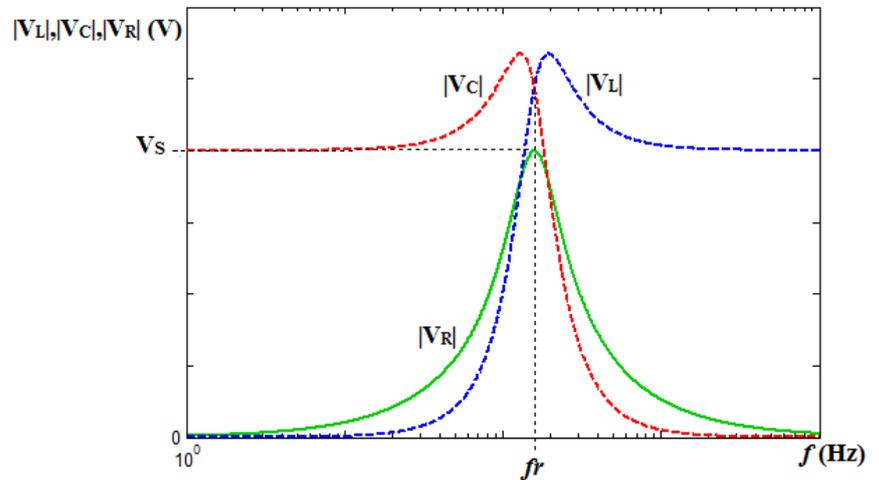


Figure (9) $|V_c|, |V_L|$ and $|V_R|$ vs. f

- Figure (10) below shows a time domain representation for all the vectors shown on the phasor diagram for the case $f < f_r$:

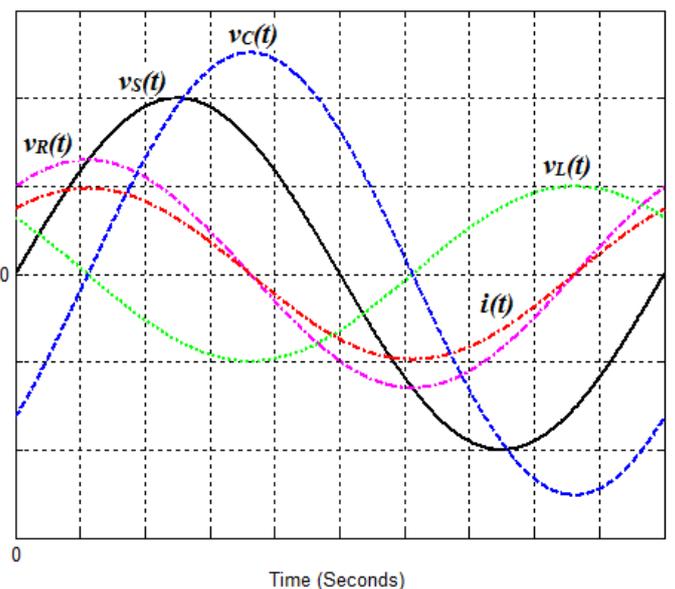


Figure (10) Series RLC Circuit Time Domain Representation