

**University of Jordan  
School of Engineering  
Electrical Engineering Department**

**EE 219  
Electrical Circuits Lab**

**EXPERIMENT 7 REPORT & PRE-LAB  
RESONANCE**

**Section # \_\_\_\_\_ Group # \_\_\_\_\_**

**Student Name**

**ID**

- 1.**
- 2.**
- 3.**
- 4.**

# EXPERIMENT 7

## RESONANCE

*Note: Use MATLAB to quickly perform theoretical calculations by defining a vector of frequencies then using array arithmetic.*

### PROCEDURE A - SERIES RESONANCE

4. What is the equation for the resonant frequency of a series RLC circuit?

.....

5. Use that above equation to find the resonant frequency in this experiment.

.....


6. What is the equation for the quality factor  $Q$ , and bandwidth  $B$  of a series RLC circuit?

.....

7. Use the proper equations to find the frequencies  $f_1$  and  $f_2$ , at which the current amplitude is approximately 0.707 times the resonant current (i.e., the half-power points).

.....

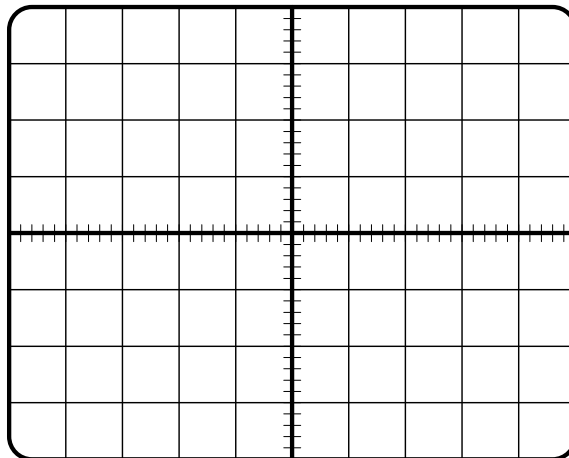9. Set the oscilloscope to work in the X-Y mode. At the frequency of 6000 Hz, draw what you see on the oscilloscope screen.



11. Draw what you see on the oscilloscope screen at the resonant frequency in the X-Y mode.

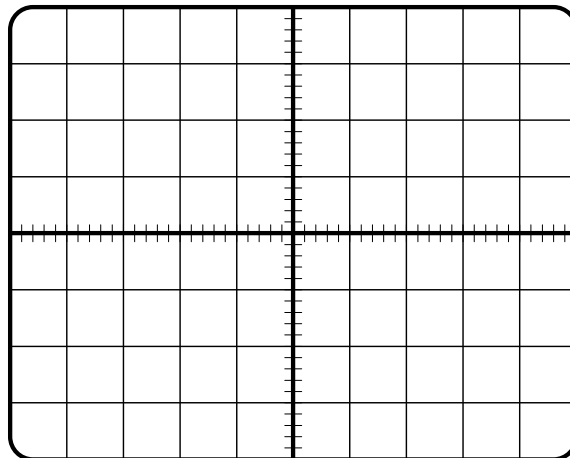


Table 1

AC Source Frequency (Hz)	$ V_S $ (peak) (V)		$V_S$ period $T$ ( $\mu$ s)		$ V_R $ (peak) (V)		$\angle V_R$ with $V_S$ (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
6000								
9000								
14400								
16800								
30000								
48000								
$f_r =$ _____								
$f_1 =$ _____								
$f_2 =$ _____								

Table 2

AC Source Frequency (Hz)	$ V_C $ (peak) (V)		$\angle V_C$ with $V_S$ (degrees)		$ V_L $ (peak) (V)		$\angle V_L$ with $V_S$ (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
6000								
9000								
14400								
16800								
30000								
48000								
$f_r =$ _____								
$f_1 =$ _____								
$f_2 =$ _____								

16. What is the relationship between the capacitor voltage  $V_C$  and inductor voltage  $V_L$  at resonant frequency?

.....

17. Consider the capacitor voltage amplitude  $|V_C|$ . Which one is higher  $|V_C|$  at resonant frequency or  $|V_C|$  below resonant frequency?

.....

18. Consider the inductor voltage phase  $\angle V_L$ . Which one is higher  $\angle V_L$  at resonant frequency or  $\angle V_L$  below resonant frequency? Note: In phase, consider the positive or negative signs.

.....

**Table 3**

AC Source Frequency (Hz)	$ I $ (peak) (mA) $= V_R/R$		$\angle I$ with $V_s$ ( $= \angle V_R$ with $V_s$ )		$ Z  =  V_s / I $ (peak/peak) (k $\Omega$ )		$\angle Z = \angle V_s - \angle I$ (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
6000								
9000								
14400								
16800								
30000								
48000								
$f_r = \underline{\hspace{2cm}}$								
$f_1 = \underline{\hspace{2cm}}$								
$f_2 = \underline{\hspace{2cm}}$								

20. Using the measured values in Table 3, plot (**by hand**) the following figures using the graph paper attached at the end of the report: (1)  $|Z|$  versus source frequency; (2)  $\angle Z$  versus source frequency; (3)  $I$  versus source frequency.

21. For the above plots, state your conclusions under the plot? Also identify the resonant frequency and bandwidth in each plot.

**PROCEDURE B -PARALLEL RESONANCE**

4. What is the equation for the resonant frequency of a parallel RLC circuit?

.....

5. Use that above equation to find the resonant frequency in this experiment.

.....

6. What is the equation for the quality factor  $Q$ , and bandwidth  $B$  of a parallel RLC circuit?

.....

7. Use the proper equations to find the frequencies  $f_1$  and  $f_2$ , at which the current amplitude is approximately  $1.414 = 1/0.707$  times the resonant current (i.e., the bandwidth limits).

.....

Table 4

AC Source Frequency (Hz)	$V_S$ (peak) (V)		$V_S$ period $T$ ( $\mu$ s)		$V_{R'}$ (peak) (V)		$\angle V_{R'}$ with $V_S$ (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
6000								
9000								
14400								
16800								
30000								
48000								
$f_r = \underline{\hspace{2cm}}$								
$f_1 = \underline{\hspace{2cm}}$								
$f_2 = \underline{\hspace{2cm}}$								

12. What is the relationship between the capacitor current  $I_C$  and inductor current  $I_L$  at resonant frequency?

.....

13. Consider the capacitor current phase  $\angle I_C$ . Which one is higher  $\angle I_C$  at resonant frequency or  $\angle I_C$  above resonant frequency? Note: In phase, consider the positive or negative signs.

.....

14. Consider the inductor current amplitude  $|I_L|$ . Which one is higher  $|I_L|$  at resonant frequency or  $|I_L|$  above resonant frequency?

.....

Table 5

AC Source Frequency (Hz)	$I$ (peak) (mA) = $V_{R'}/R'$		$\angle I$ with $V_s$ (= $\angle V_{R'}$ with $V_s$ )		$ Y  =  I / V_s $ (peak/peak) (mS)		$\angle Y = \angle I - \angle V_s$ (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
6000								
9000								
14400								
16800								
30000								
48000								
$f_r =$ _____								
$f_1 =$ _____								
$f_2 =$ _____								

16. Using the *measured* values in Table 5, plot (**by hand**) the following figures using the graph paper attached at the end of the report: (1)  $|Y|$  versus source frequency; (2)  $\angle Y$  versus source frequency; (3)  $I$  versus source frequency.

17. For the above plots, state your conclusions under the plot? Also identify the resonant frequency and bandwidth in each plot.

Table 6

AC Source Frequency (Hz)	$ S $ (mVA)	$\angle S$ (degrees)	$P$ (mW)	$Q$ (mVAR)	$PF$ value	$PF$ lead or lag
	Measured	Measured	Measured	Measured	Measured	Measured
6000						
9000						
14400						
16800						
30000						
48000						
$f_r =$ _____						
$f_1 =$ _____						
$f_2 =$ _____						

19. Using the values in Table 6, plot (**by hand**) the following figure using the graph paper attached at the end of the report:  $P$  and  $Q$  on the same plot versus source frequency.

20. For the above plot, state your conclusions under the plot?

21. At what frequency the real power  $P$  is minimum? Why?

.....

22. At what frequency the magnitude of the reactive power  $|Q|$  is maximum? Why?

.....

### CONCLUSIONS

Summarize in clear but concise format what you learned from this experiment:

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

**\*\* End \*\***

