

**University of Jordan
School of Engineering
Electrical Engineering Department**

**EE 219
Electrical Circuits Lab**

**EXPERIMENT 8
DELTA-WYE CONVERSION**

Prepared by: Dr. Mohammed Hawa

EXPERIMENT 8 DELTA-WYE CONVERSION


OBJECTIVE

This experiment investigates the Δ -Y and Y- Δ impedance conversion, and how can this be used to simplify the analysis of DC and AC circuits.

DISCUSSION

Delta-Wye and Wye-Delta Conversion

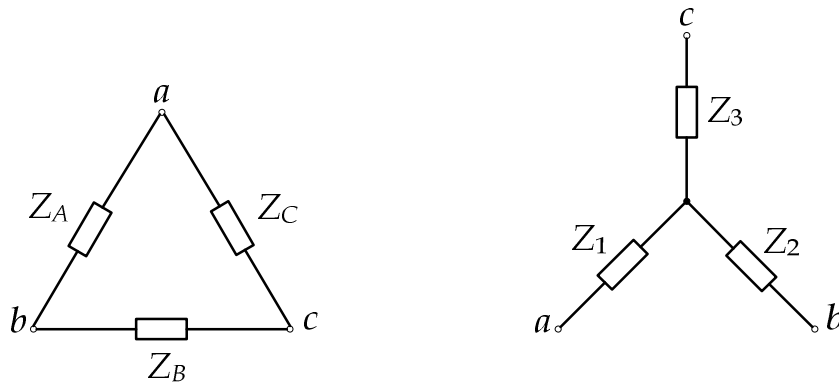The following two impedance connections are electrically equivalent, because both result in the same voltage values across the three nodes a , b and c .



To convert from the Y configuration to the Δ configuration, we use the following equations:

$$Z_A = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_B = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

Hence, the general rule is:

$$Z_{\Delta} = \frac{\text{sum of pairwise products of } Z_Y \text{'s}}{\text{the opposite } Z_Y}$$

And to convert from Δ to Y, we use the following equations:

$$Z_1 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$$

$$Z_2 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$$

$$Z_3 = \frac{Z_C Z_A}{Z_A + Z_B + Z_C}$$

Hence, the general rule is:


$$Z_Y = \frac{\text{product of adjacent } Z_{\Delta}'s}{\text{sum of } Z_{\Delta}'s}$$

If all the impedances are equal, the equations reduce to the following simple form:

$$Z_{\Delta} = 3 \times Z_Y$$


$$Z_Y = \frac{1}{3} \times Z_{\Delta}$$

The Δ -Y and Y- Δ impedance conversion is useful in many cases to quickly analyze circuits that otherwise require a more complex nodal or mesh analysis. An example is shown below, where a Δ -Y transformation of the left circuit to the right one allows us to apply a simple current divider to find the currents in R_D and R_E resistances, or to find the equivalent resistance between nodes a and d using parallel and series rules.

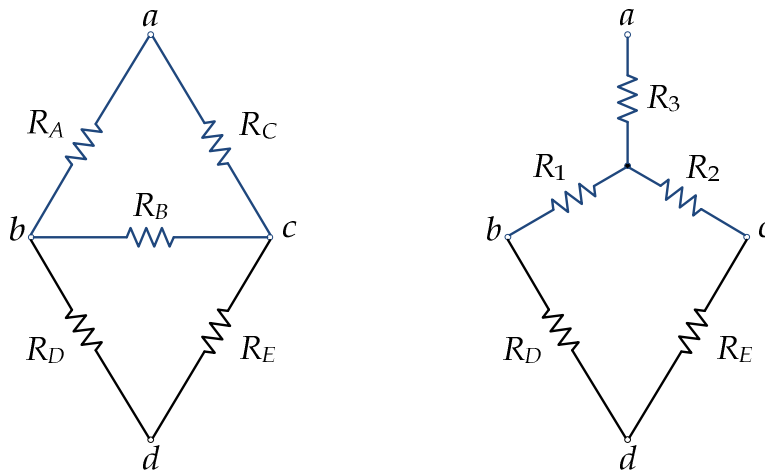

PROCEDURE A - Y-Δ TRANSFORMATION

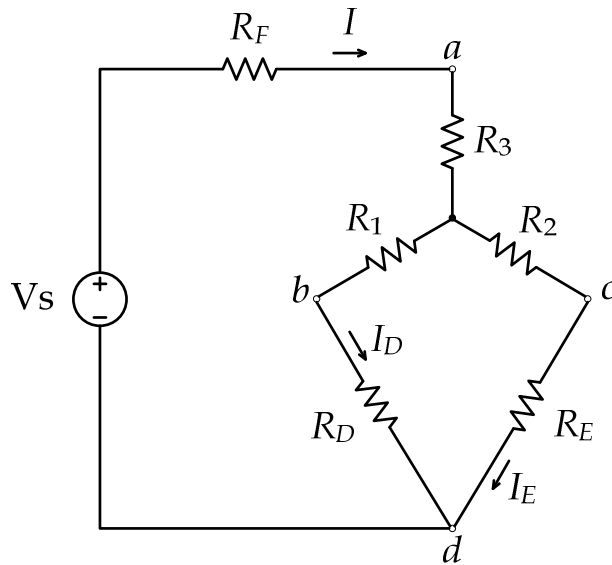1. Construct the circuit shown below. Assume that $R_1 = 1000 \Omega$, $R_2 = 3000 \Omega$, $R_3 = 1710 \Omega$, $R_D = 1600 \Omega$, $R_E = 820 \Omega$, and $R_F = 2200 \Omega$. The resistor R_3 can be built using a 510Ω resistor in series with another 1200Ω resistor.



2. Set the DC supply output voltage control to minimum then connect it to the circuit. Switch the DC supply ON, and set its voltage to $V_S = 8$ Volts. Verify this voltage using a voltmeter.

3. Use the current divider rule to calculate the theoretical currents I , I_D , and I_E and also to evaluate the theoretical voltages V_{ad} , V_{bd} , and V_{cd} . Record your answers in the theory part of Tables 1 and 2.

4. Using a voltmeter, measure the voltages V_{ad} , V_{bd} , and V_{cd} , and record the values in Table 1. Pay attention to polarity.

Table 1

V_{ad} (V)		V_{bd} (V)		V_{cd} (V)	
Theory	Meas.	Theory	Meas.	Theory	Meas.

5. Use an ammeter to measure the DC currents I , I_D , and I_E , and record the values in Table 2. Pay attention to polarity.


Table 2

I (mA)		I_D (mA)		I_E (mA)	
Theory	Meas.	Theory	Meas.	Theory	Meas.

6. Convert the Y connection in the above circuit (represented by R_1 , R_2 , and R_3) into a Δ connection, and draw the resulting circuit below.

.....

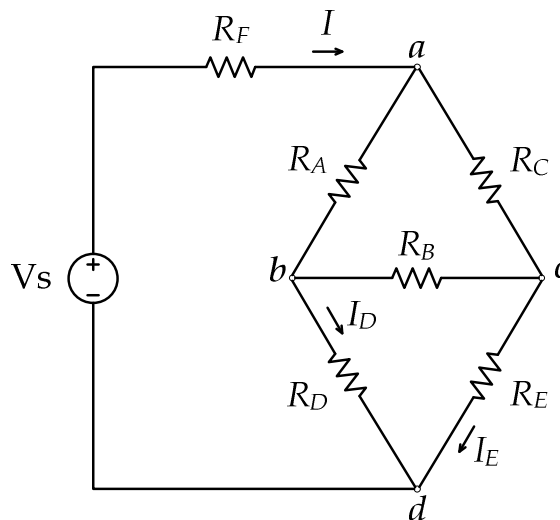7. Now construct the circuit shown below. Assume that $R_A = 3300 \Omega$, $R_B = 5600 \Omega$, $R_C = 10000 \Omega$, $R_D = 1600 \Omega$, $R_E = 820 \Omega$, and $R_F = 2200 \Omega$.



8. Set the DC supply output voltage control to minimum then connect it to the circuit. Switch the DC supply ON, and set its voltage to $V_s = 8$ Volts. Verify this voltage using a voltmeter.

9. How is this circuit different than the equivalent circuit you sketched in part 6 above?

.....

10. Use nodal or mesh analysis in the above circuit to calculate the theoretical voltages V_{ad} , V_{bd} , and V_{cd} and theoretical currents I , I_D , and I_E . Record your answers in the theory part of Tables 3 and 4.

11. Using a voltmeter, measure the voltages V_{ad} , V_{bd} , and V_{cd} , and record the values in Table 3. Pay attention to polarity.

Table 3

V_{ad} (V)		V_{bd} (V)		V_{cd} (V)	
Theory	Meas.	Theory	Meas.	Theory	Meas.

12. Use an ammeter to measure the DC currents I , I_D , and I_E , and record the values in Table 4. Pay attention to polarity.

Table 4

I (mA)		I_D (mA)		I_E (mA)	
Theory	Meas.	Theory	Meas.	Theory	Meas.

13. Are the results in Tables 1 and 2 close to the values in Tables 3 and 4?


.....

14. Why are the values in Tables 1 and 2 not exactly the same as the values in Tables 3 and 4?

.....

PROCEDURE B - Δ -Y TRANSFORMATION

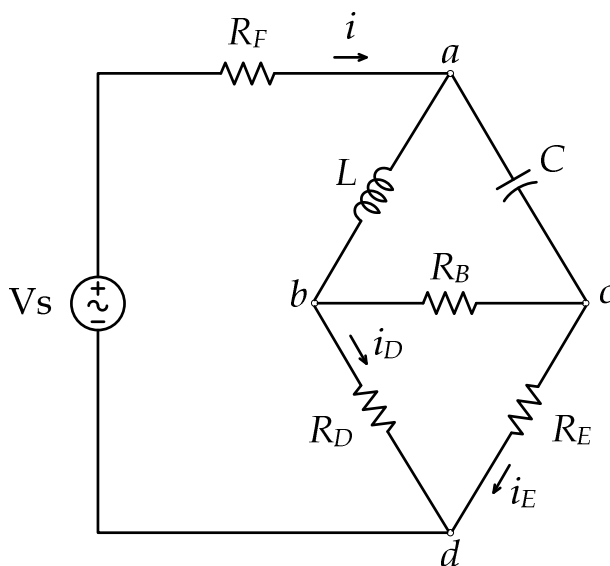1. Construct the circuit shown below. Assume that $L = 10$ mH, $C = 2.2$ μ F, $R_B = 10000$ Ω , $R_D = 680$ Ω , $R_E = 2200$ Ω , and $R_F = 100$ Ω .



2. Set the function generator to produce a sinusoidal waveform (AC) with frequency of 10000 Hz, and *peak voltage* of $V_p = 3$ V.

CAUTION: Some older function generators have a defect and produce an AC signal with a slight DC shift. Hence, if you do not see a symmetric sinusoidal signal above and below zero volts, adjust the DC offset knob slightly to force a zero DC offset in the function generator output.

3. Use theoretical Δ -Y transformation of L , C and R_B to evaluate the currents I_D and I_E in the circuit, and also the voltages V_{bd} and V_{cd} and record the answers in Tables 5 and 6 at the different frequencies shown in the tables. Make sure to evaluate both magnitude and phase for each complex quantity.

4. Draw the equivalent circuit after you did the Δ -Y transformation for the frequency 10000 Hz.

.....

5. Use the oscilloscope to measure the peak values of the voltages V_{bd} and V_{cd} and their phase shifts compared to V_s . Remember that you can change the horizontal sweep setting of the oscilloscope to make more accurate measurements of the phase. Record the measurements in Table 5, then evaluate the currents I_D and I_E and record the answers in Table 6.

CAUTION: Whenever you change the frequency of the function generator, verify the period of the signal from the oscilloscope to get accurate readings. Also re-check the peak-to-peak voltage as the function generator might change the amplitude when you change the frequency.

6. Where did you place the oscilloscope channel probes when measuring V_{bd} ?

.....

Table 5

AC Source Frequency (Hz)	V_{bd} (peak) (V)		$\angle V_{bd}$ with V_s (degrees)		V_{cd} (peak) (V)		$\angle V_{cd}$ with V_s (degrees)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
10000								
60000								

Table 6

AC Source Frequency (Hz)	I_D (peak) (mA) $= V_{bd}/R_D$		$\angle I_D$ with V_s ($= \angle V_{bd}$ with V_s)		I_E (peak) (mA) $= V_{cd}/R_E$		$\angle I_E$ with V_s ($= \angle V_{cd}$ with V_s)	
	Theory	Meas.	Theory	Meas.	Theory	Meas.	Theory	Meas.
10000								
60000								

7. Does changing the frequency affect the answers in the above tables? Why?

.....

**** End ****