

**University of Jordan
School of Engineering
Electrical Engineering Department**

**EE 219
Electrical Circuits Lab**

**EXPERIMENT 9 REPORT & PRE-LAB
TRANSFER FUNCTION
OF TWO-PORT NETWORKS**

Section # _____ Group # _____

Student Name

ID

- 1.
- 2.
- 3.
- 4.

EXPERIMENT 9

TRANSFER FUNCTION OF TWO-PORT NETWORKS

Note: Use MATLAB to quickly perform theoretical calculations by defining a vector of frequencies then using array arithmetic.

PROCEDURE A - RESISTIVE TWO-PORT NETWORK

4. What is the theoretical equation for the transfer function $|H(f)|$ in the above circuit?

.....

5. Is the above equation dependent on frequency or not?

.....

Table 1

AC Source Frequency (kHz)	$ V_{in} $ (peak) (V)		$ V_{out} $ (peak) (V)		$ H(f) = V_{out} / V_{in} $	
	Theory	Meas.	Theory	Meas.	Theory	Meas.
0.43						
2.9						
4.3						
17						
57						
96						
120						
140						
1900						

8. Using the measured values in Table 1, plot (**by hand** using the graph paper attached at the end of the report) the transfer function $|H(f)|$ versus source frequency.

9. For the above plot, state your conclusions under the plot?

PROCEDURE B - LOW-PASS FILTER TWO-PORT NETWORK

4. What is the theoretical equation for the transfer function $|H(f)|$ in the above circuit?

.....

5. Is the above equation dependent on frequency or not?

.....

6. What is the equation for the cut-off frequency f_c of the first order RC circuit shown above?

.....

7. Use the above equation to find the frequency f_c , at which the output voltage is approximately 0.707 times the maximum possible output voltage (i.e., the half-power point). Record this value below. **Then** use the oscilloscope to determine this cutoff frequency experimentally by observing the frequency at which the output voltage is approximately 0.707 times the maximum. Record this *experimental* frequency in Table 2.

.....

Table 2

AC Source Frequency (kHz)	$ V_{in} $ (peak) (V)		$ V_{out} $ (peak) (V)		$ H(f) = V_{out} / V_{in} $	
	Theory	Meas.	Theory	Meas.	Theory	Meas.
0.43						
4.3						
57						
76						
96						
120						
130						
140						
1900						
$f_c = \underline{\hspace{2cm}}$						

10. Using the measured values in Table 2, plot (**by hand** using the graph paper attached at the end of the report) the transfer function $|H(f)|$ versus source frequency.

11. For the above plot, state your conclusions under the plot? Also identify the cut-off frequency in the plot.

PROCEDURE C - HIGH-PASS FILTER TWO-PORT NETWORK

4. What is the theoretical equation for the transfer function $|H(f)|$ in the above circuit?

.....

5. Is the above equation dependent on frequency or not?

.....

6. What is the equation for the cut-off frequency f_c of the first order RC circuit shown above?

.....

7. Use the above equation to find the frequency f_c , at which the output voltage is approximately 0.707 times the maximum possible output voltage (i.e., the half-power point). Record this value below. **Then** use the oscilloscope to determine this cutoff frequency experimentally by observing the frequency at which the output voltage is approximately 0.707 times the maximum. Record this *experimental* frequency in Table 3.

.....

Table 3

AC Source Frequency (kHz)	$ V_{in} $ (peak) (V)		$ V_{out} $ (peak) (V)		$ H(f) = V_{out} / V_{in} $	
	Theory	Meas.	Theory	Meas.	Theory	Meas.
0.43						
2.9						
4.3						
5.8						
17						
37						
57						
560						
1900						
$f_c = \underline{\hspace{2cm}}$						

10. Using the measured values in Table 3, plot (**by hand** using the graph paper attached at the end of the report) the transfer function $|H(f)|$ versus source frequency.

11. For the above plot, state your conclusions under the plot? Also identify the cut-off frequency in the plot.

PROCEDURE D - BANDPASS FILTER TWO-PORT NETWORK

4. What is the theoretical equation for the transfer function $|H(f)|$ in the above circuit?

.....

5. Is the above equation dependent on frequency or not?

.....

6. What are the equations for the two cut-off frequencies of the above ladder circuit?

.....

7. Use the above equations to find the frequencies, at which the output voltage is approximately 0.707 times the maximum possible output voltage (i.e., the half-power points). Record these values below. **Then** use the oscilloscope to determine such cutoff frequencies experimentally by observing the frequency at which the output voltage is approximately 0.707 times the maximum. Record these *experimental* frequencies in Table 4.

.....

10. Using the measured values in Table 4, plot (**by hand** using the graph paper attached at the end of the report) the transfer function $|H(f)|$ versus source frequency.

11. For the above plot, state your conclusions under the plot? Also identify the two cut-off frequencies in the plot.

Table 4

AC Source Frequency (kHz)	$ V_{in} $ (peak) (V)		$ V_{out} $ (peak) (V)		$ H(f) = V_{out} / V_{in} $	
	Theory	Meas.	Theory	Meas.	Theory	Meas.
0.43						
4.3						
5.8						
37						
57						
76						
120						
130						
1900						
$f_{c1} = \underline{\hspace{2cm}}$						
$f_{c2} = \underline{\hspace{2cm}}$						

CONCLUSIONS

Summarize in clear but concise format what you learned from this experiment:

.....

.....

.....

.....

.....

.....

.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....

**** End ****







