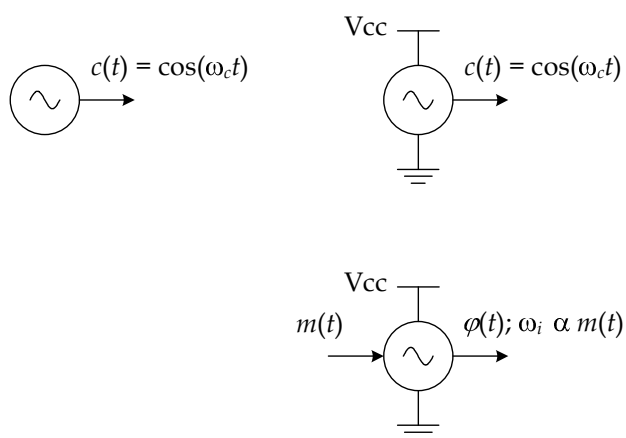


# Lecture 16: FM Modulators and Demodulators

Dr. Mohammed Hawa  
Electrical Engineering Department  
University of Jordan

EE421: Communications I: Lecture 16. For more information read Chapter 5 in your textbook or visit <http://wikipedia.org/>.

## FM Modulator: VCO



# Oscillator


- To build an oscillator, we require three components:
  - Amplifier
  - Positive feedback
  - LC tank
- The frequency of the oscillator is controlled by the LC tank resonant circuit.
- Many implementations available: Colpitts oscillator, Hartley oscillator, Ring oscillator, etc.

Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan

3
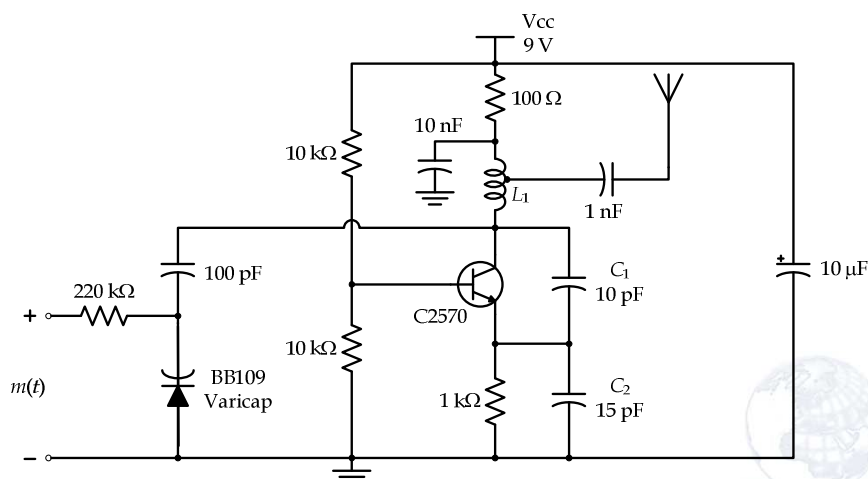
## Example VCO: uses Colpitts oscillator (NOT in the exam)



Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan

4

## FM Demodulators

- FM Discriminator (also called Slope Detector or Ratio Detector):
  - Convert frequency variations into amplitude variations, then use an envelope detector.
- Quadrature Detector:
  - Convert frequency variations into phase variations, then use a phase-difference detector.
- Phase-Locked Loop:
  - A phase-difference feedback system.





Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan

5

## FM Discriminator

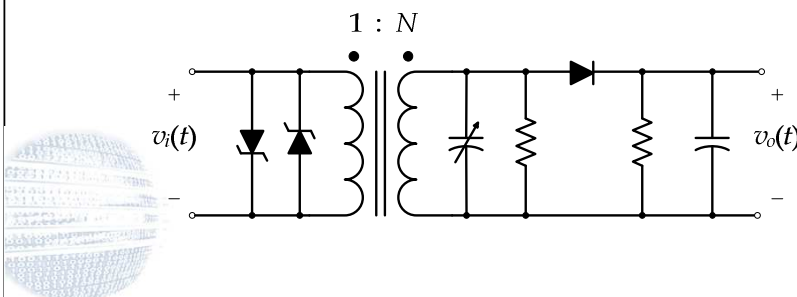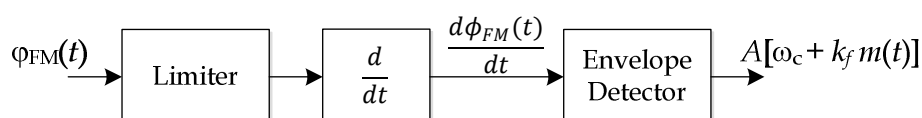

Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan

6

## (FM) into (FM+AM)


Copyright © Dr. Mohammed Hawa
Electrical Engineering Department, University of Jordan
7

$|H(\omega)|$

$\angle H(\omega)$

Copyright © Dr. Mohammed Hawa
Electrical Engineering Department, University of Jordan
8

## Quadrature Detector

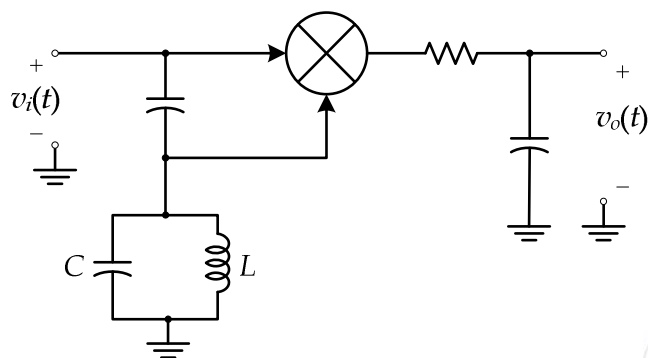


Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan

9

## Phase-Locked Loop (PLL)

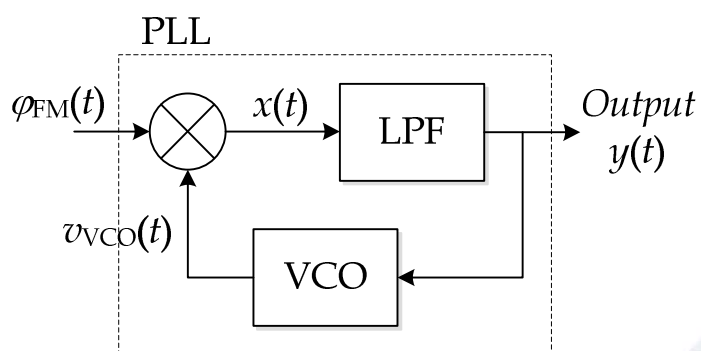

Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan

10

## PLL Terminology


- A PLL is said to be **in-lock** if the frequency of the inner VCO  $v_{VCO}(t)$  is exactly the *same* as the frequency of the received signal  $v_{in}(t) = \varphi_{FM}(t)$ .
- If the PLL stays in-lock, then the output voltage  $v_{out}(t)$  is proportional to the baseband message signal  $m(t)$ .
- We want the PLL to stay in-lock.
- See the datasheet for MC4046 for details.



Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan 11


## PLL: Step 1 (In Lock)

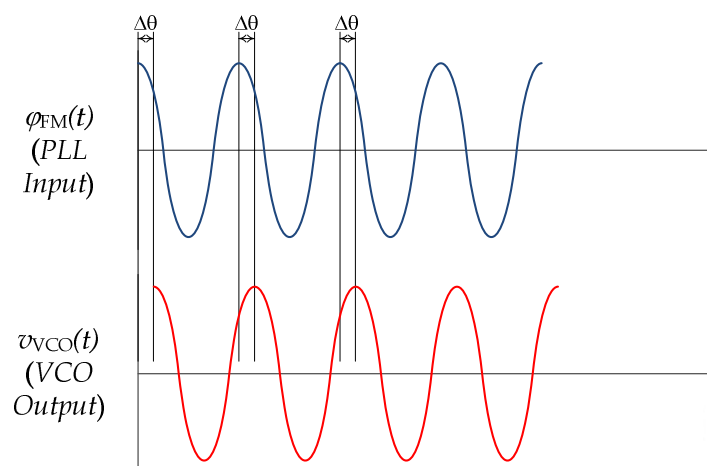

Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan 12


## PLL: Step 2 (Input changes)

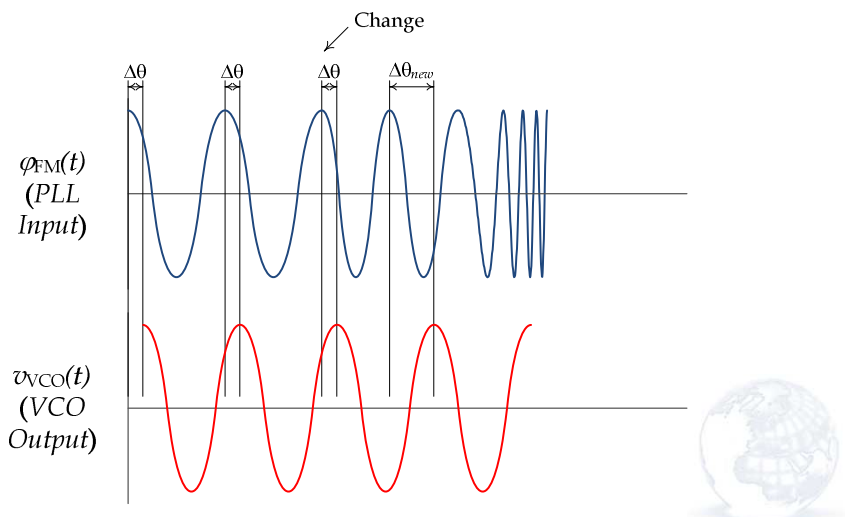

Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan 13

## PLL: Step 3 (PLL follows)

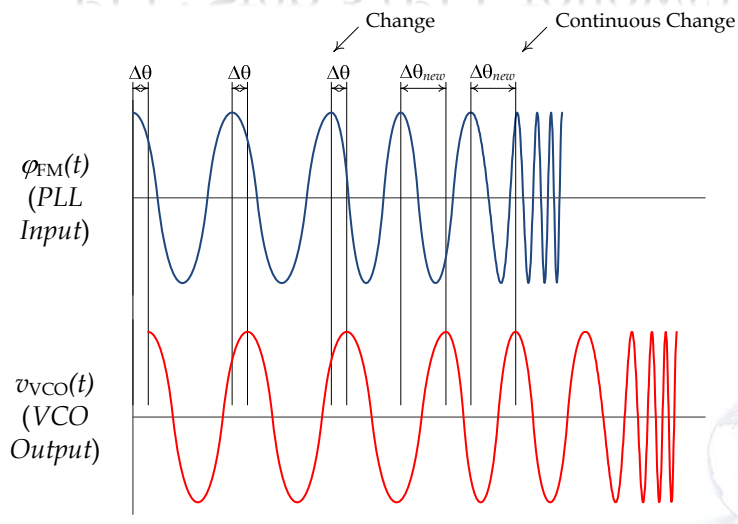

Copyright © Dr. Mohammed Hawa

Electrical Engineering Department, University of Jordan 14

## PLL Applications


- Carrier recovery for Synchronous detectors.
- Clock recovery for digital baseband receivers.
- Stabilizing VCO frequencies in FM transmitters.
- FM Demodulator.



Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan 15

## PM Demodulator: Synchronous

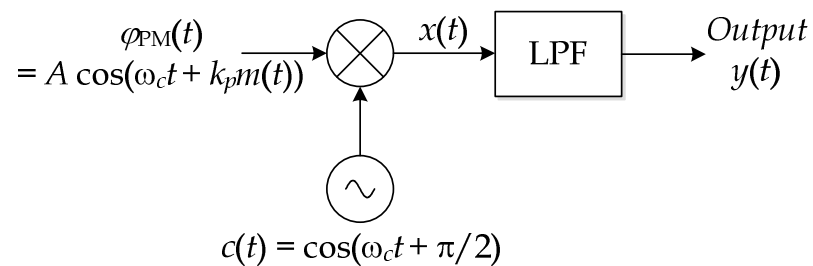

Copyright © Dr. Mohammed Hava

Electrical Engineering Department, University of Jordan 16