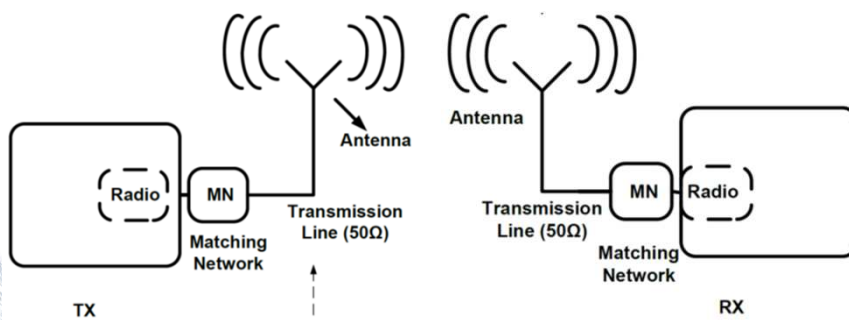


Lecture 11: Antennas & Antenna Matching

Prof. Mohammed Hawa
Electrical Engineering Department
The University of Jordan

EE423: Communication Electronics

Antenna for Wireless Transmission



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

2

Antenna Types & Length


- Wire Antenna
- PCB Antenna or Microstrip Antenna
- Panel Antenna
- Patch Antenna
- Phased Array Antenna
- Chip Antenna
- Antenna length is related to transmitted signal wavelength λ

$$\lambda = \frac{c}{f}$$




Dipole Antenna

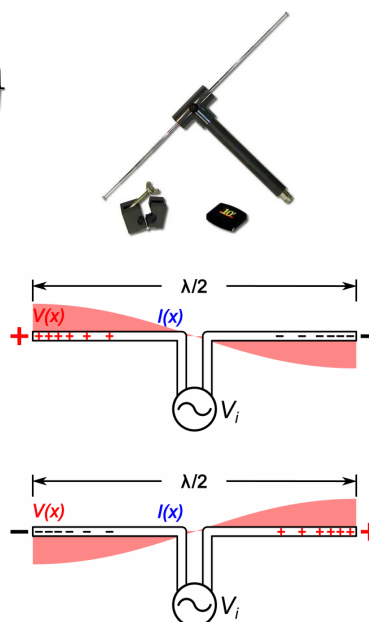- Consists of two identical conductive elements.
- Each side of the transmitter feedline is connected to one of the conductors.
- Build variable electric field from potential difference.



EM Signal Propagation

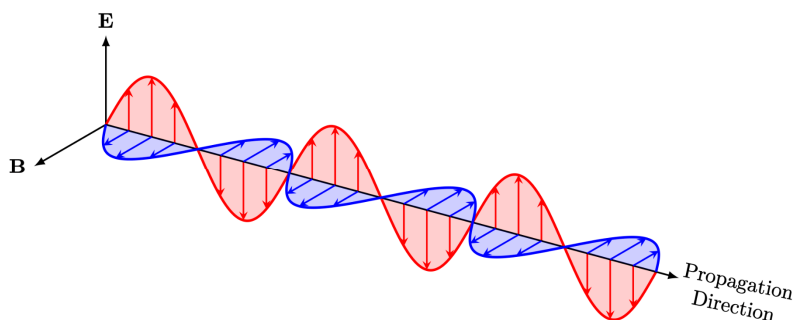


- Variable electric field induces magnetic field, which induces electric field, thus building a propagating EM signal.

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

5

Radiation Pattern

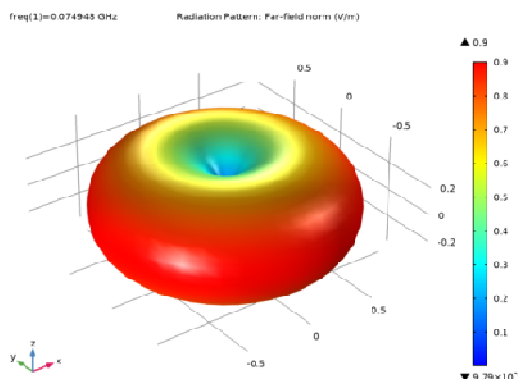


- Radiation pattern shows the directional (angular) dependence of the strength of the radio waves from the antenna.

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

6

Radiation Pattern Views

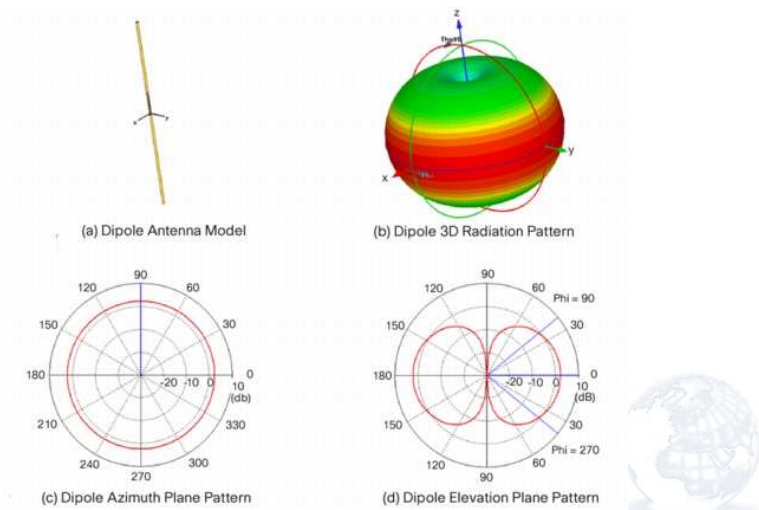



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

7

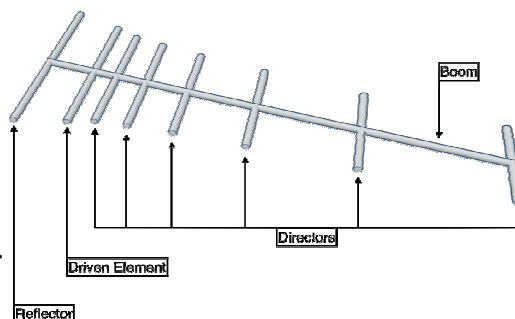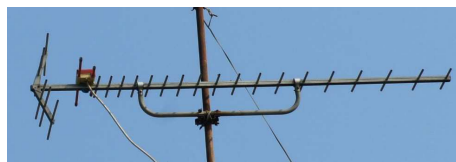Example: UHF TV Antenna

- **Yagi-Uda** antenna uses a dipole for its driven element.
- Used to receive terrestrial TV transmission in UHF range.
- UHF (Ultra High Frequency): 300 MHz to 3 GHz.
- Directional antenna.



Copyright © Prof. Mohammed Hawa


Electrical Engineering Department, The University of Jordan

8


Radiation Pattern




(a) Yagi Antenna Model

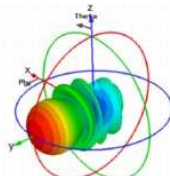

(b) Yagi Antenna 3D Radiation Pattern

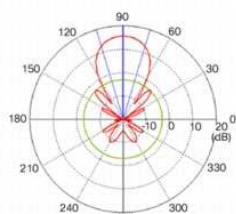

(c) Yagi Antenna Azimuth Plane Pattern

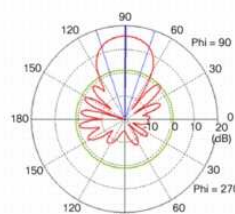

(d) Yagi Antenna Elevation Plane Pattern




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

9

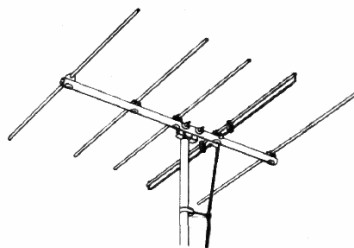Example: VHF TV Antenna

- For VHF range, which requires a longer dipole, many Yagi-Uda antennas use a folded dipole design for the driven element.
- VHF (Very High Frequency): 30 MHz to 300 MHz.
- But *not* always: see Rabbit Ears TV Antenna.



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

10

Also for HF & FM Transmitters




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

11

Monopole Antenna

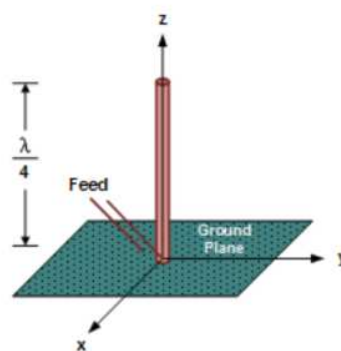- Straight conductor mounted perpendicularly over conductive surface (ground plane).
- The driving signal from the transmitter goes through a feedline.
- One side of the feedline is attached to the lower end of the monopole, and the other side is attached to the ground plane (consisting of cables buried under Earth).




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

12

Ground Provides Mirror Image

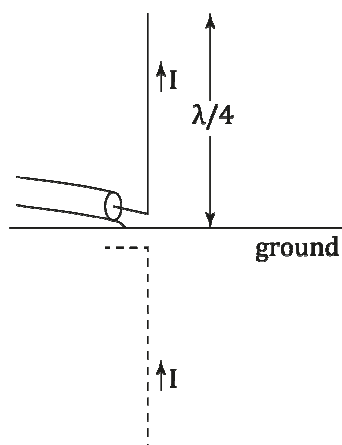- A $\lambda/4$ monopole antenna and its ground image combined form a $\lambda/2$ dipole that radiates only in the upper half of space.



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

13

Example: AM Radio

- AM radio station mast radiator monopole antenna.
- The mast itself is connected to the transmitter and radiates the radio waves.
- It is mounted on a ceramic insulator to isolate it from the ground.




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan


14

Radiation Pattern

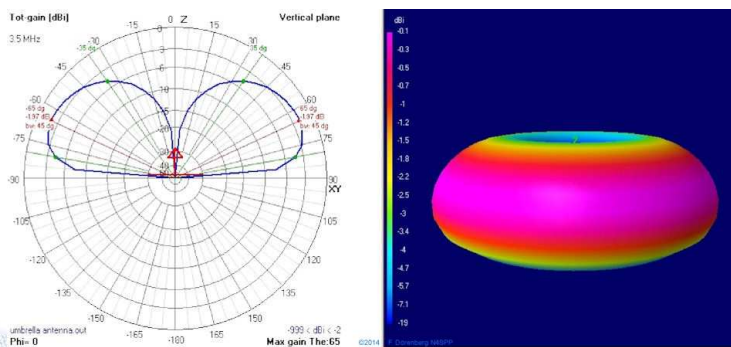

- Vertical radiation pattern of ideal monopole antenna over a perfect infinite ground.

Variation on Radiation Pattern

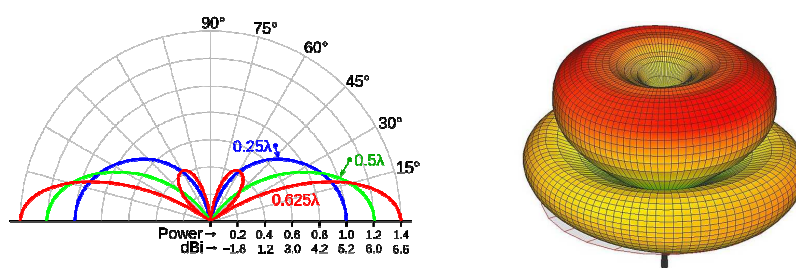

- Vertical radiation patterns of monopole antennas with different lengths.
- Multi-lobed radiation pattern for 0.625λ monopole.

Examples: FM Radio, Car, WiFi AP




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

17

AM vs. FM Antenna

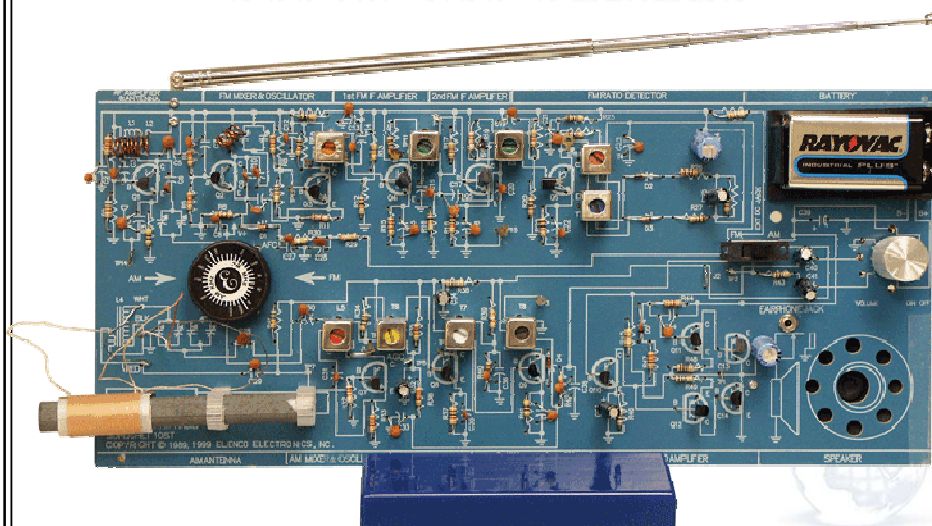

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

18

Dish Antenna

- The dish itself is just a concentrator or reflector.
- Example: Satellite TV.
- The signal is highly attenuated.



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

19

PCB Antenna

- Trace drawn on the PCB.
- Can be a straight trace, inverted F-type trace, meandered trace, circular trace, or a curve with wiggles depending on the antenna type and space constraints.
- PCB antenna requires more PCB area, has a lower efficiency than the wire antenna, but is cheaper and easier to manufacture.
- Acceptable for low-range applications, e.g. Bluetooth.



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

20

PCB Antenna



Inverted F




Meander Line Inverted-F




Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan


21

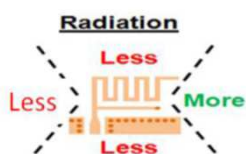


About Z axis

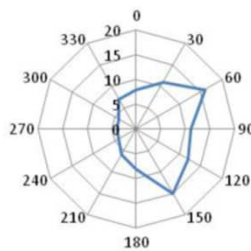

About X axis

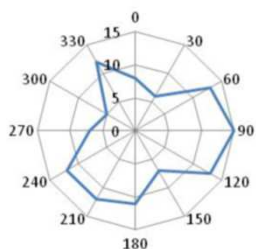

About Y axis



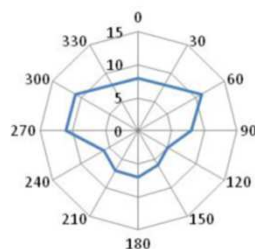


Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

22

Example: Mouse, Keyboard, Sensor

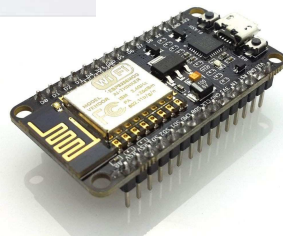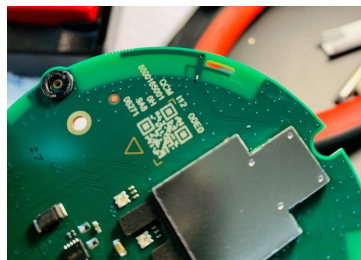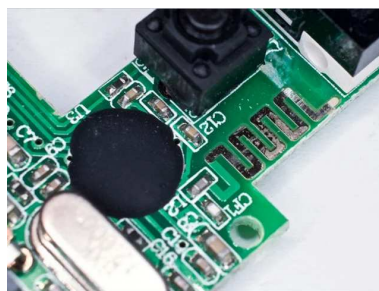


Copyright © Prof. Mohammed Hawa


Electrical Engineering Department, The University of Jordan

23

Different Shapes Possible

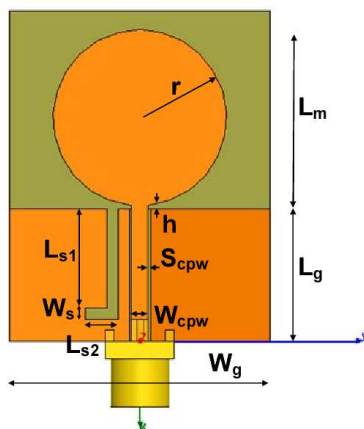

(a)

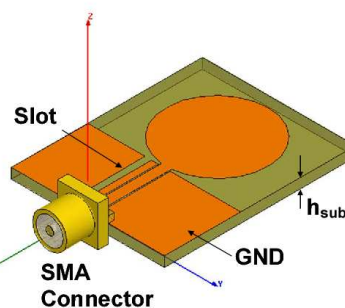

(b)

Copyright © Prof. Mohammed Hawa


Electrical Engineering Department, The University of Jordan

24


Panel Antennas



Cellular Telephony & TV UHF

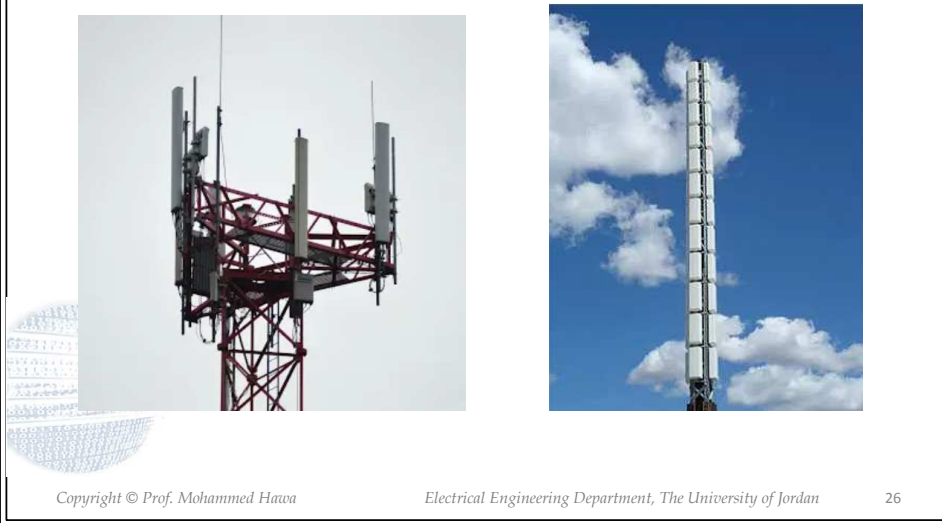

Patch Antennas

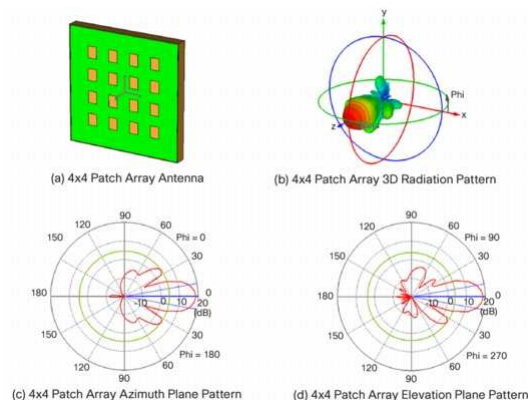

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

27

Phased Array Antenna


- Computer-controlled array of antennas to build a beam of radio waves that can be electronically steered to point in different directions without moving the antennas.
- Transmitted signal is fed to individual antenna elements with proper phase for each so output from the separate elements combine (superpose) to increase power radiated in desired directions and suppress radiation in undesired directions.
- Examples: Starlink satellite system (from SpaceX), 5G MIMO for cell phones.

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

28

Computer Controls Phase Shifters

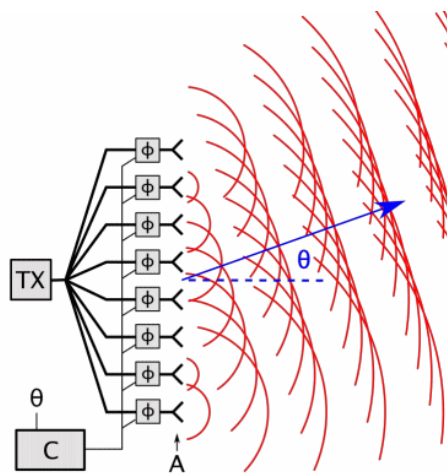


Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

29

Starlink Dish

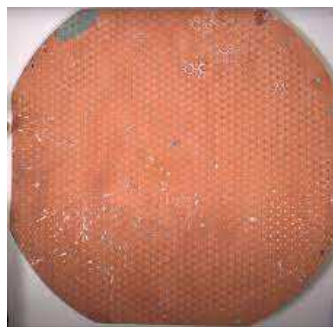



Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan


30

Chip Antennas

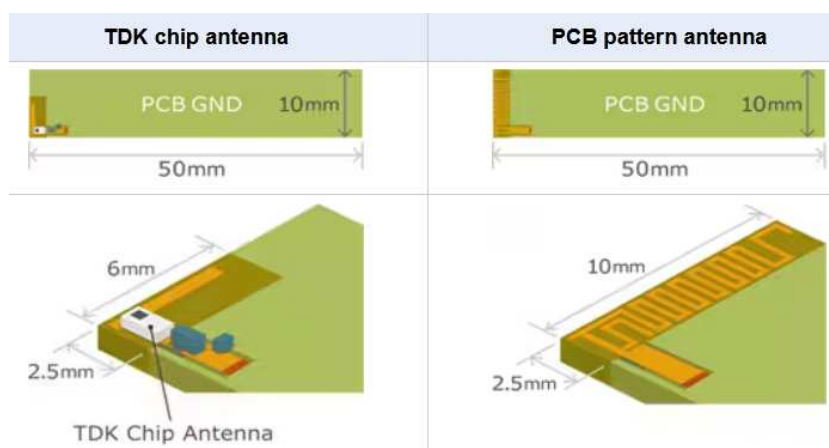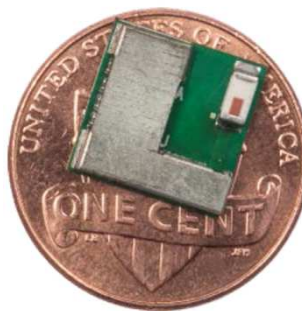- Antenna inside the IC itself, with a conductor packed inside.
- Useful when there is limited space to print a PCB antenna or support a 3D wire antenna.




Antenna Design

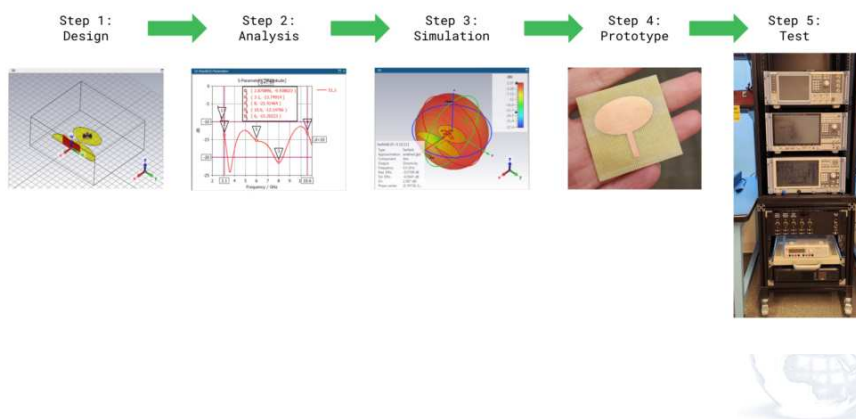

Antenna Matching

- For maximum power transfer, we need:

$$Z_{in} = Z_S^*$$

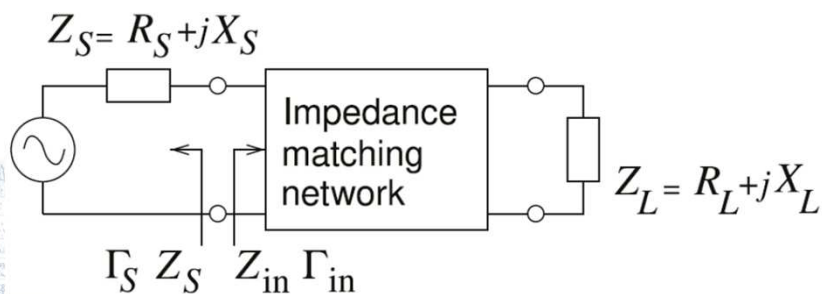

Matching Network

- If load has non-zero real part (i.e., can dissipate power), a matching network can always be found.
- Design of matching network is called impedance matching.
- Matching networks are constructed using lossless elements, such as lumped capacitors, lumped inductors, transmission lines, microstrips, etc. So, ideally, there is no extra power loss in the circuit.




Elements for Matching Networks

- Up to few GHz, lumped inductors and lumped capacitors can be used.
- Above a few GHz, lumped inductors are not recommended, due to high loss (wire resistance) and high parasitic capacitances (inter-winding capacitance).
- Lumped inductors can be replaced with segments of transmission lines or stubs (they suffer smaller loss and have smaller parasitics).
- Lumped capacitors can still be used at higher frequencies compared to lumped inductors.
- Transmission lines cannot be used at lower frequencies because they need to be longer due to the longer signal wavelength λ .



Lumped Inductors

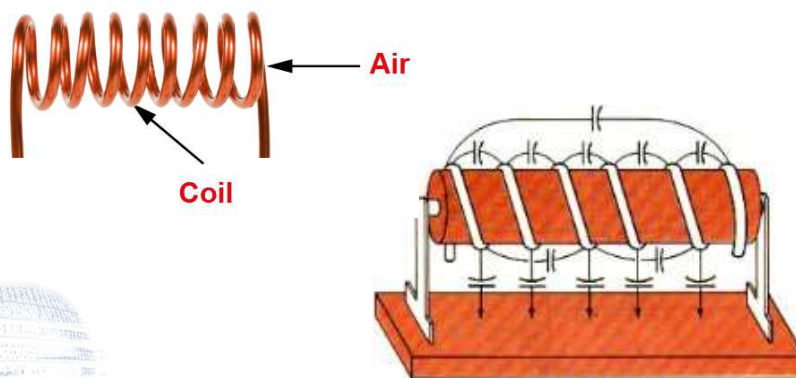


Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

37

Matching Network

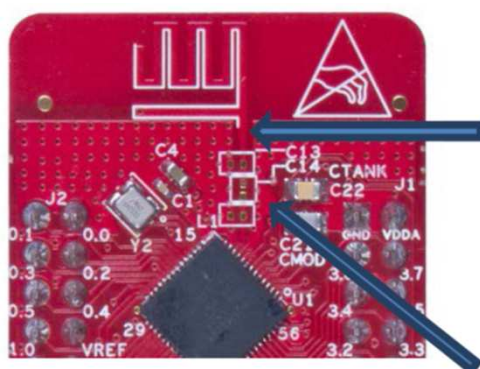

Only 3 mm trace to Antenna. Transmission line width is not critical


Matching Network

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

38

Examples for Stubs

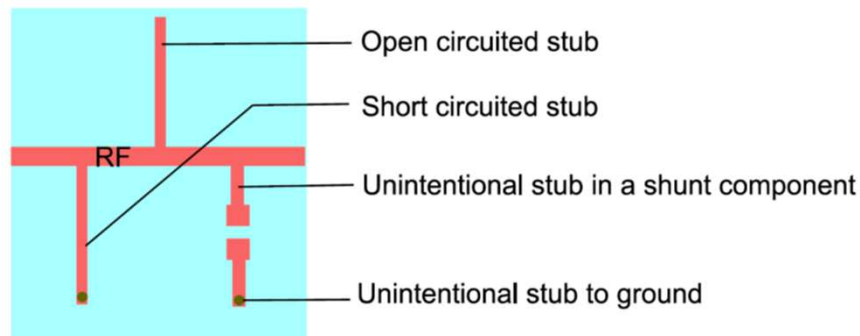

Copyright © Prof. Mohammed Hawa

Electrical Engineering Department, The University of Jordan

39

Controlling Q factor


- With L network (i.e., two-element matching), the circuit Q is fixed once source and load resistances, R_S and R_L , are fixed.
- Introducing a third element in the matching network provides an extra degree of freedom in the design for adjusting Q , and hence bandwidth.
- Popular three-element matching networks are the T network and the Pi network.

Copyright © Prof. Mohammed Hawa


Electrical Engineering Department, The University of Jordan

40

Three-Element Matching

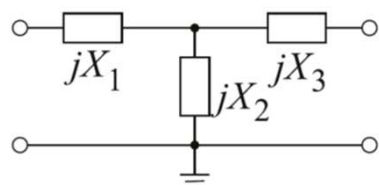

(a) T network

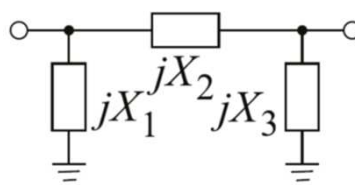

(b) Pi network

Matching Via Smith Chart

